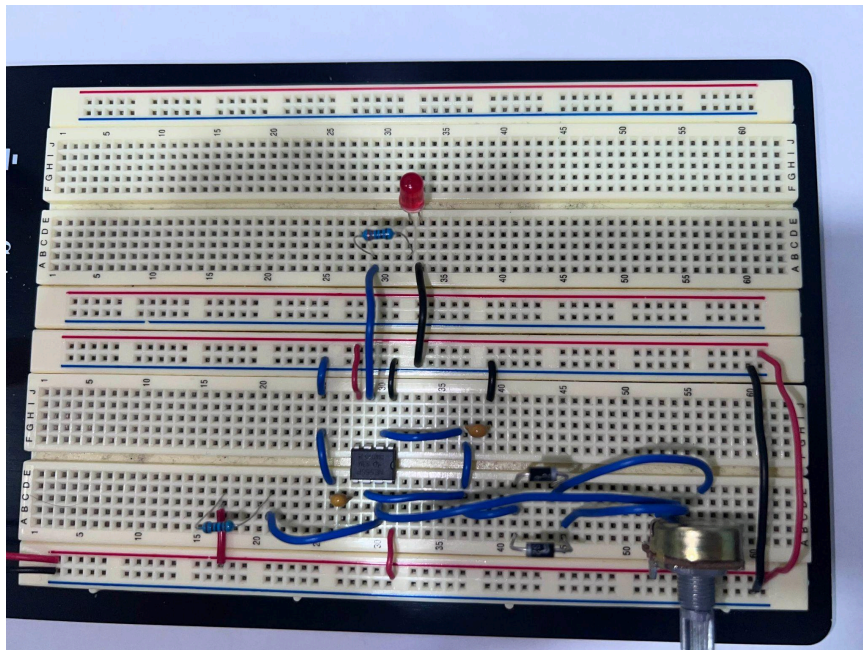


# Analog PWM LED Controller – Design Explanation and Analysis

## Overview


This project focuses on the design and implementation of a variable duty cycle Pulse Width Modulation (PWM) generator used for LED dimming. Unlike digital systems that rely on microcontrollers, this system utilizes an NE555 timer in an astable configuration, modified with steering diode logic to provide precise analog control over the output signal.


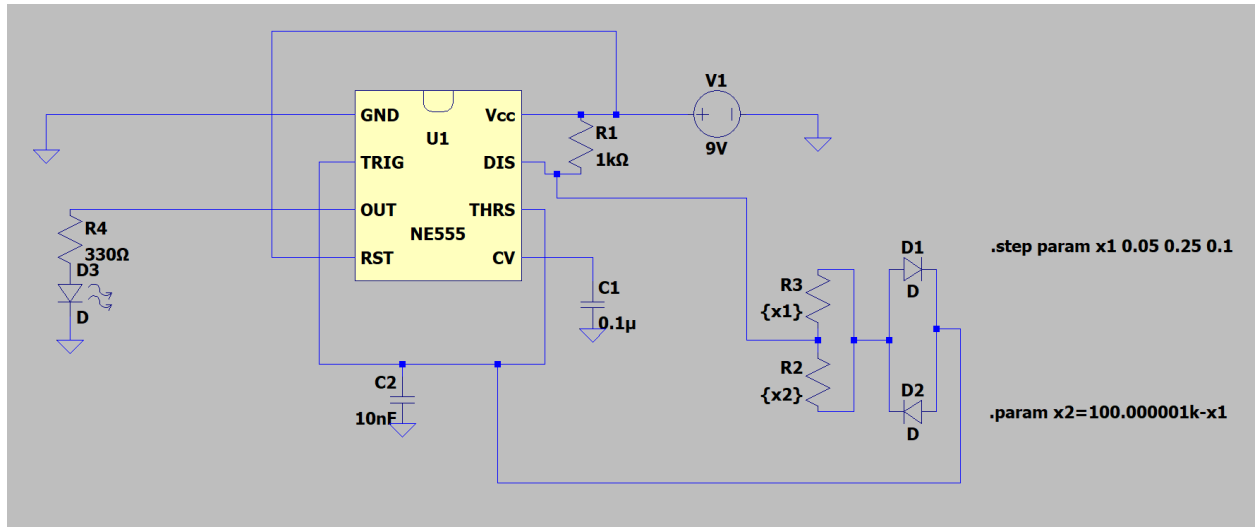
## Design Approach


The core of the circuit is an NE555 timer IC. In a standard astable circuit, the charge and discharge paths of the timing capacitor share the same resistors, making it difficult to achieve a variable duty cycle without changing the frequency. To solve this, this design utilizes:

- **Steering Diode Logic:** Two **1N4007 diodes** are used to isolate the charging and discharging paths.
- **Variable Resistance:** A **100kΩ potentiometer** allows the user to manually adjust the ratio of the charge to discharge time, effectively changing the duty cycle.
- **Timing Capacitor:** A **10 nF ceramic capacitor** was selected to set a high frequency oscillation, ensuring the PWM switching is invisible to the human eye.
- **Power Regulation:** The circuit is stabilized by an **LM7805 voltage regulator**, converting a 12V source into a steady 5V DC rail to protect the timing components from voltage fluctuations.


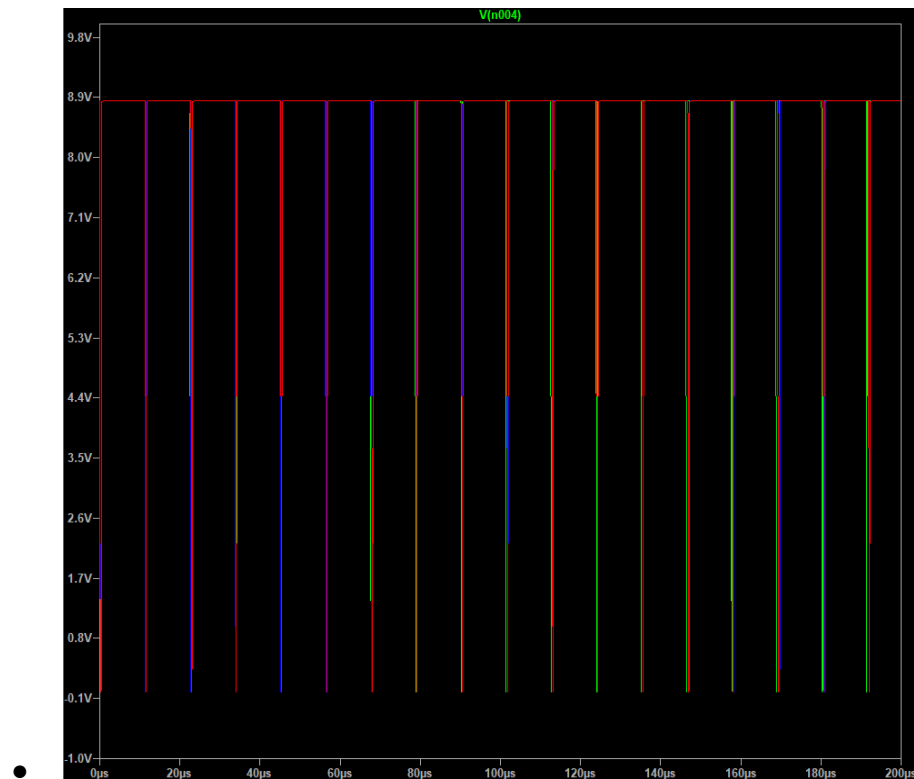
## This Method:

- **Decouples Control:** Independent charge/discharge paths allow for a duty cycle range of **5% to 95%** while keeping frequency relatively stable.
- **Reduces Component Stress:** A **1kΩ protection resistor** was integrated into the discharge path to prevent high current spikes through the IC during rapid switching.
- **Validation:** All timing constants and transient behaviors were verified in **LTspice** prior to breadboarding to ensure system reliability.



## Trade-offs

The decision to use the NE555 timer with steering diodes was a deliberate design choice balancing:

- **Hardware Efficiency:** Minimizing the IC count by using the 555 timer's internal flip flops for switching.
- **Control Range:** Achieving a near full range of dimming (5-95%) which is often difficult in standard 555 astable circuits.
- **Circuit Complexity:** The diode steering method is simpler to debug and requires fewer external passive components than Op Amp based PWM generators.

## Conclusion

This project demonstrates the effectiveness of utilizing discrete analog components to solve common power control challenges. By exploring **steering diode logic** and validating designs through **LTspice**, I successfully developed a stable and efficient dimming system. This project provided a strong foundation in high frequency circuit design and component level optimization, reinforcing a deeper understanding of analog timing fundamentals.